

Ring Oscillator Simulation

ELEC 654 – Advanced Simulation of Electronic Circuits

ÖNDER GÖRMEZ

171021012

I. Introduction

- A ring oscillator comprises of an odd number of CMOS inverters. The output of each inverter is used as input for the next one. The last output is feedback to the first inverter. Because of the delay time of each stage the whole circuit spontaneously starts oscillating at a certain frequency. The frequency f depends on the number of stages n and the delay time of the inverters τ as follows. [1]

$$f = \frac{1}{2n\tau}$$

II. Details

- A real ring oscillator only requires power to operate. Above a certain threshold voltage, oscillations begin spontaneously. To increase the frequency of oscillation, two methods are commonly used. Firstly, the applied voltage may be increased. This increases both the frequency of the oscillation and the current consumed. The maximum permissible voltage applied to the circuits limits the speed of a given oscillator. Secondly, making the ring from a smaller number of inverters results in a higher frequency of oscillation given a certain power consumption. [2]

III. Operation

- To understand the operation of a ring oscillator, one must first understand gate delay. In a physical device, no gate can switch instantaneously. In a device fabricated with MOSFETs, for example, the gate capacitance must be charged before current can flow between the source and the drain. Thus, the output of every inverter in a ring oscillator changes a finite amount of time after the input has changed. From here, it can be easily seen that adding more inverters to the chain increases the total gate delay, reducing the frequency of oscillation. [2]


IV. Jitter

- Period of ring oscillator vibrates in a random manner $T = T + T'$ where T' is a random value. In high-quality circuits, the range of T' is relatively small compared to T . This variation in oscillator period is called jitter. Local temperature effects cause the period of a ring oscillator to wander above and below the long-term average period. When the local silicon is cold, the propagation delay is slightly shorter, causing the ring oscillator to run at a slightly higher frequency, which eventually raises the local temperature. When the local silicon is hot, the propagation delay is slightly longer, causing the ring oscillator to run at a slightly lower frequency, which eventually lowers the local temperature. [2]


V. Applications

- The **voltage-controlled oscillator (VCO)** in most **phase-locked loops (PLL)** is built from a ring oscillator.
- Jitter of ring oscillators is commonly used in **hardware random number generators**.
- Many wafers include a ring oscillator as part of the **scribe line test structures**. They are used during wafer testing to measure the effects of manufacturing **process variations**.
- Ring oscillators can also be **used to measure the effects of voltage and temperature** on a chip. [2]


VI. Simulation on LTspice

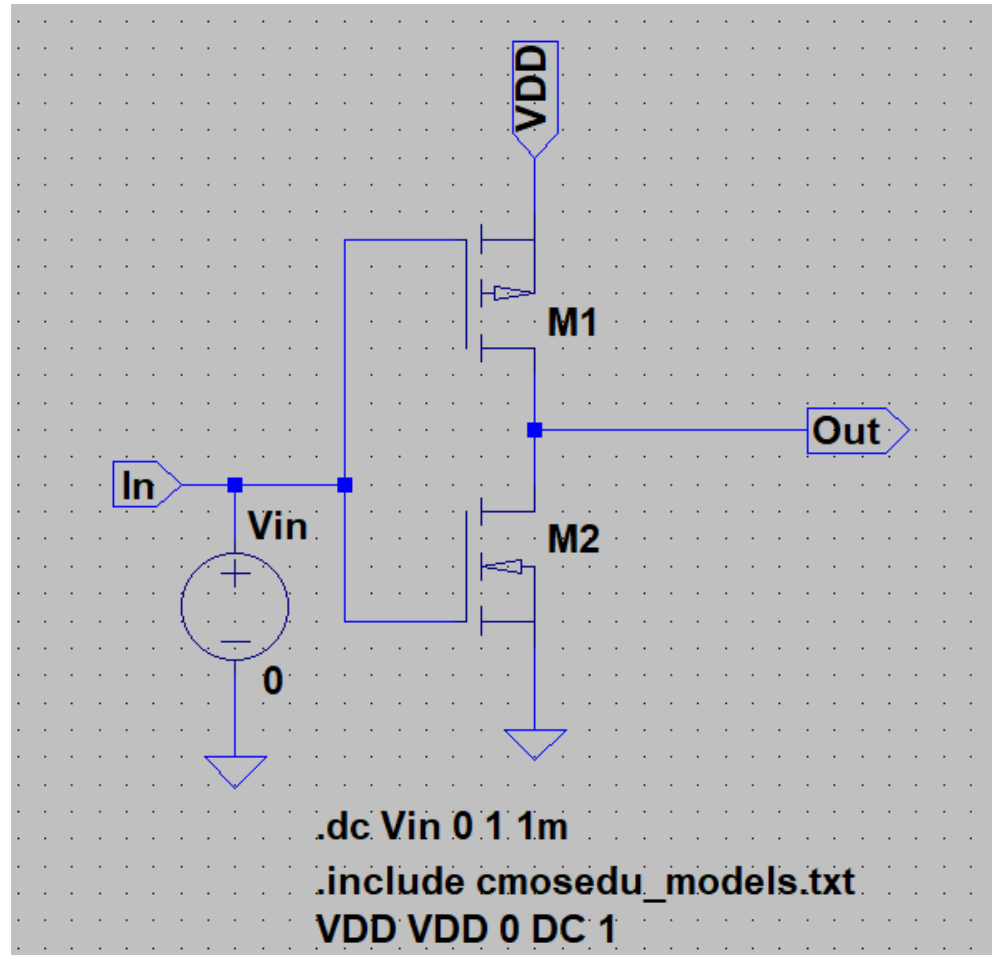


VI. Simulation on LTspice

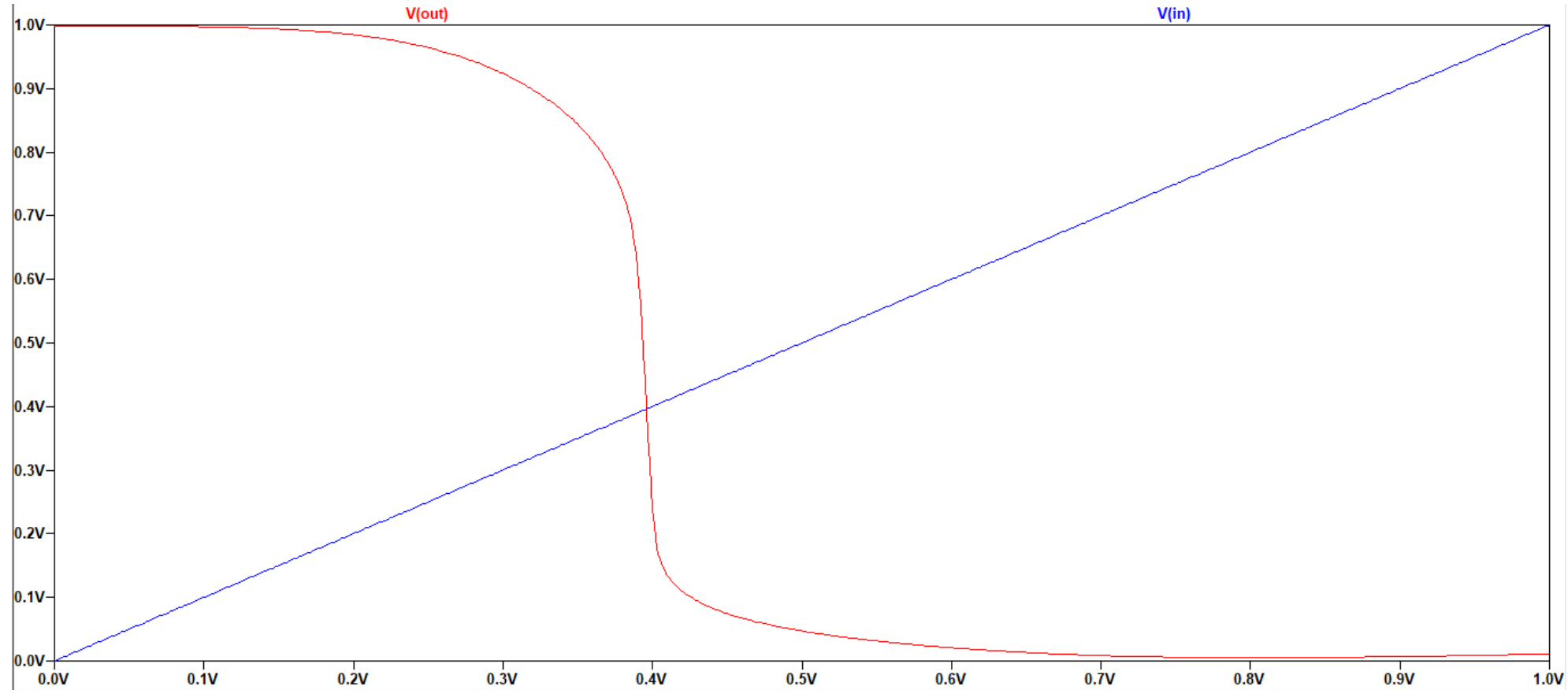


VI. Simulation on LTspice

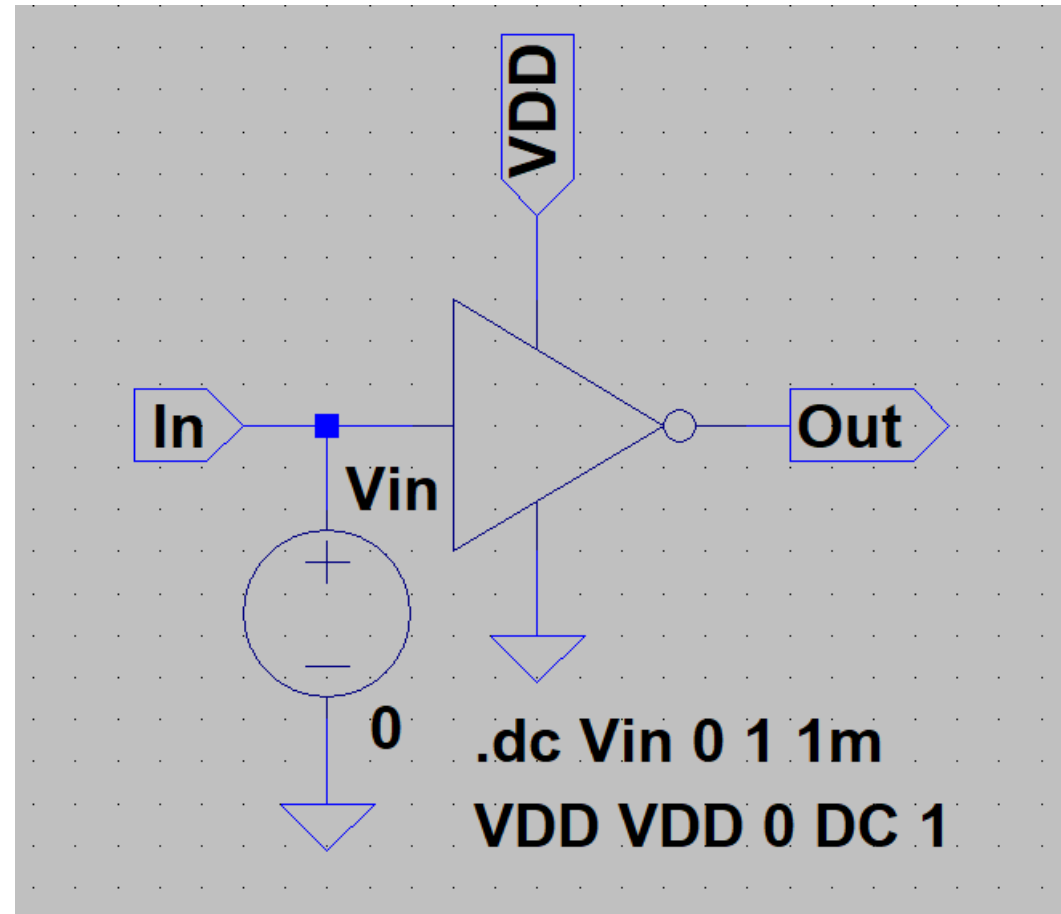


VI. Simulation on LTspice

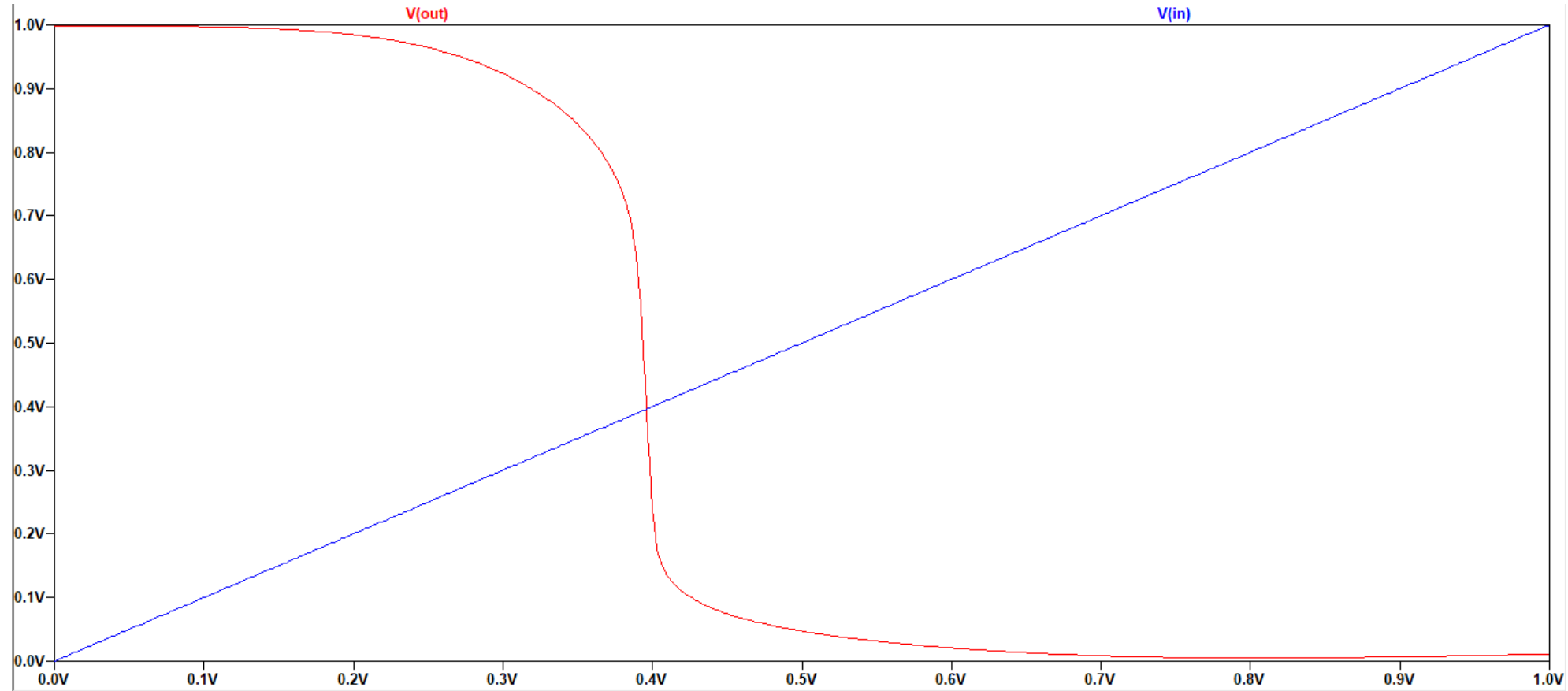

VI. Simulation on LTspice

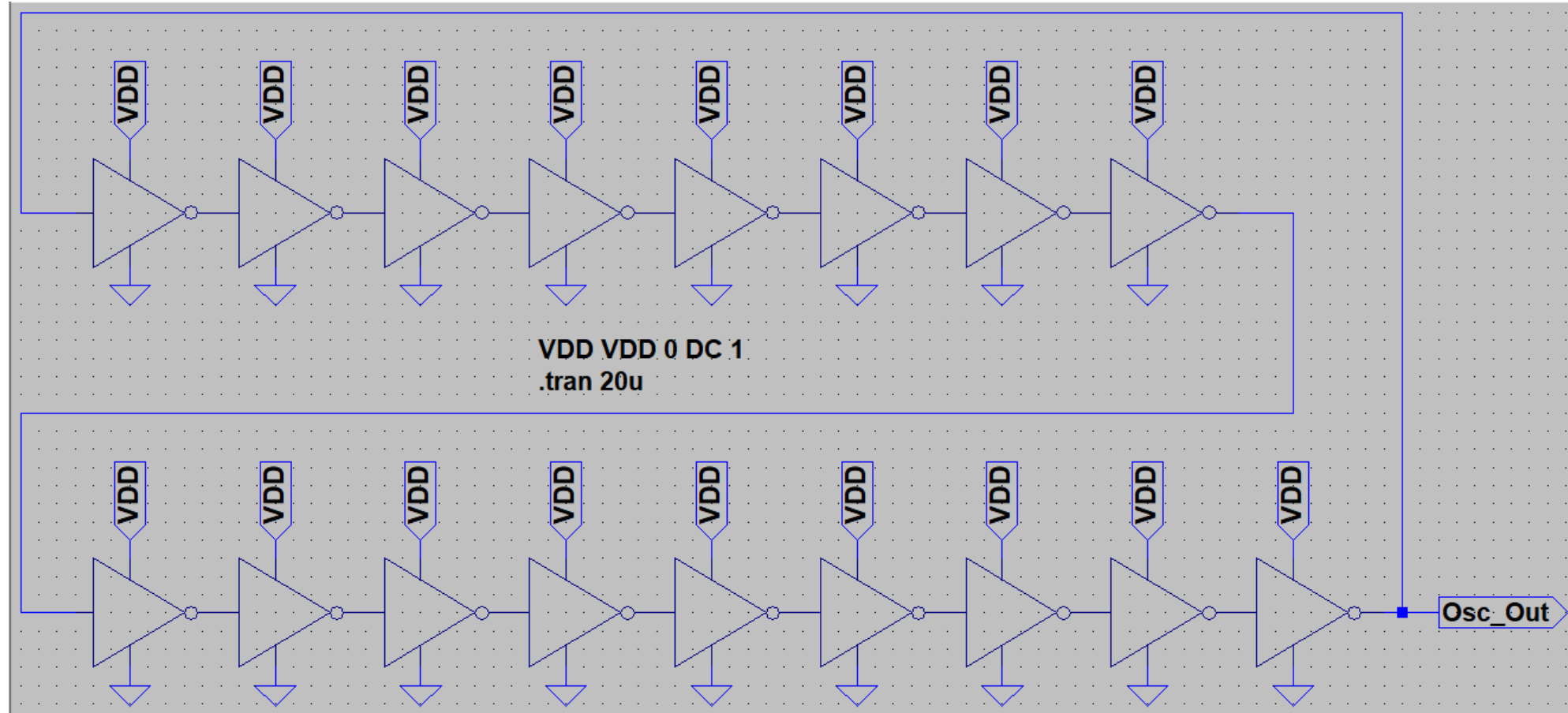


VI. Simulation on LTspice

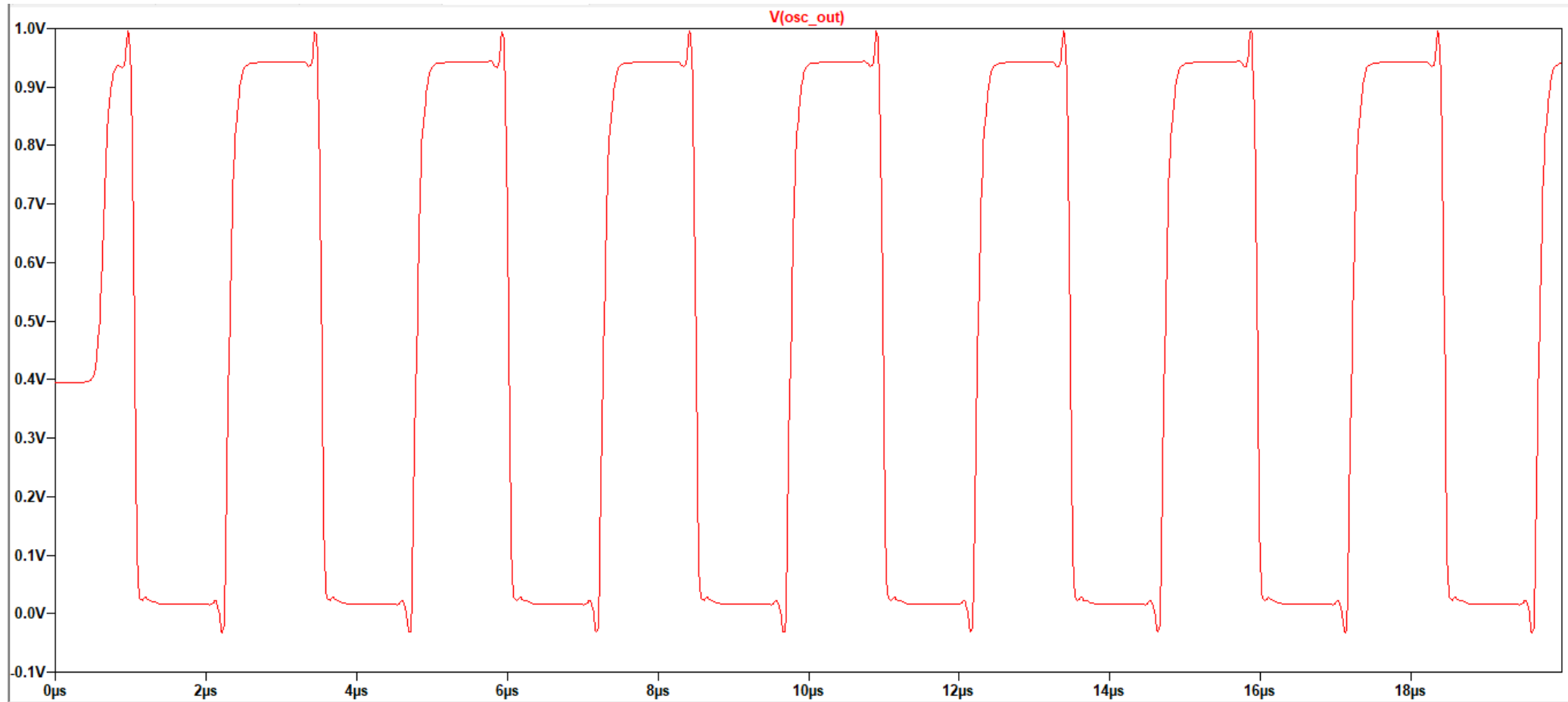

VI. Simulation on Ngspice

```
RingOscillator.cir x
1 Ring Oscillator Design
2
3 *
4 * Independent Voltage Source
5 *
6 VDD NVDD GND DC 1
7
8 *
9 * Inverter Sub Circuit Definition
10 *
11 .SUBCKT INVERTER IN OUT VDD DGND
12 .include cmosedu_models.txt
13 M1 OUT IN VDD VDD P_50n
14 M2 OUT IN DGND DGND N_50n
15 .ENDS INVERTER
16
17 *
18 *
19 * Ring oscillator circuit consisting
20 * of 17 inverters.
21 *
22 X01 Osc_Out IN02 NVDD GND INVERTER
23 X02 IN02 IN03 NVDD GND INVERTER
24 X03 IN03 IN04 NVDD GND INVERTER
25 X04 IN04 IN05 NVDD GND INVERTER
26 X05 IN05 IN06 NVDD GND INVERTER
27 X06 IN06 IN07 NVDD GND INVERTER
28 X07 IN07 IN08 NVDD GND INVERTER
29 X08 IN08 IN09 NVDD GND INVERTER
30 X09 IN09 IN10 NVDD GND INVERTER
31 X10 IN10 IN11 NVDD GND INVERTER
32 X11 IN11 IN12 NVDD GND INVERTER
33 X12 IN12 IN13 NVDD GND INVERTER
34 X13 IN13 IN14 NVDD GND INVERTER
35 X14 IN14 IN15 NVDD GND INVERTER
36 X15 IN15 IN16 NVDD GND INVERTER
37 X16 IN16 IN17 NVDD GND INVERTER
38 X17 IN17 Osc_Out NVDD GND INVERTER
39
40 *
41 * The following features must be set for the Ngspice simulation
42 * to have the same properties as LTSpice simulation.
43 *
44 .OPTIONS GMIN=1e-012 ABSTOL=1e-012 RELTOL=0.001
45 + CHGTOL=1e-014 VOLTOL=1e-006 TRTOL=1
46 + SSTOL=0.001 MINDELTA GMIN=0.0001 METHOD=trap
47 + ACCT LIST NODE OPTS
48
49 *
50 * Use initial condition if oscillation does
51 * not start.
52 *
53 *.NODESET V(NVDD)=1 V(Osc_Out)=0.71
54 *.IC V(NVDD)=1 V(Osc_Out)=0.71
55 *.TRAN 0 20us 0 20us UIC
56 .TRAN 0 20us 0 20us
57
58 *
59 * Control statement for running simulation and
60 * plotting the Osc_Out result
61 *
62 .control
63 echo *****
64 echo *** Ring Oscillator Simulation Started ***
65 echo *****
66 run
67 *print V(Osc_Out)
68 gnuplot RingOscillator V(Osc_Out) title "Ring Oscillator Output"
69 + xlabel "Time (s)" ylabel "Voltage (V)"
70 echo *****
71 echo *** Ring Oscillator Simulation Finished ***
72 echo *****
73 .endc
74
75 .END
```

VI. Simulation on Ngspice

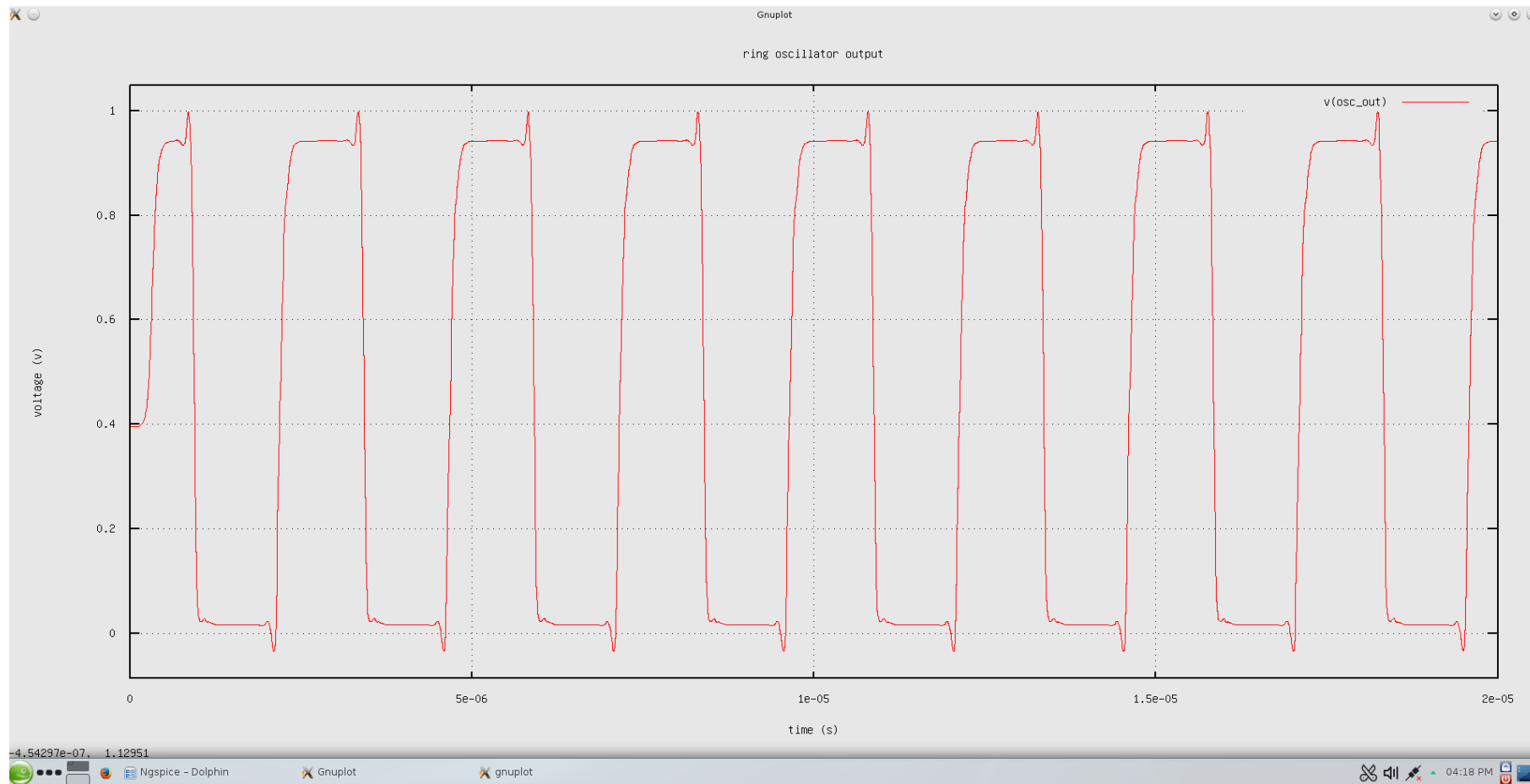

VII. References

- [1] <http://www.iue.tuwien.ac.at/phd/entner/node35.html>
- [2] https://en.wikipedia.org/wiki/Ring_oscillator
- [3] <http://cmosedu.com/>
- [4] <https://www.youtube.com/watch?v=7ShqMMWj-WI&list=PLZuGFJzpFksCaPBHdNqThrkAiQ5AyY4SJ&index=4>
- [5] <http://ngspice.sourceforge.net/docs/ngspice-manual.pdf>

THANK YOU FOR LISTENING...